

SI100B


Introduction to Information Science and Technology (Electrical Engineering)

Lecture #3 (Digital) Combinational Logic Circuits

Instructor: Junrui Liang (梁俊睿)

Oct. 8th, 2021

The Theme Story

 

(Pictures are from the Internet)


Study Purpose of Lecture #3

- 哲学 (bao'an) 三问
 - Who are you?
 - Where are you from?
 - Where are you going?

To answer those questions
throughout your life



 - In this lecture, we ask
 - How many categories of circuits are there?
 - Why digital circuits 数字电路 won in computation & communication?
 - How to build combinational logic circuits 组合逻辑电路?



Lecture Outline


1. Circuit categories 电路种类
2. Boolean logic 布尔逻辑
3. Logic gates 逻辑门电路
4. Combinational logic circuit 组合逻辑电路
 - Example: majority circuit 投票选举电路实例

----- (break) -----


5. Combinational Logic Circuits Design 组合逻辑电路设计
 - Boolean algebra 布尔代数
 - Truth table 真值表
 - Karnaugh map 卡诺图
 - Example: decoder design 解码器设计实例

Four typical circuit categories


- Passive 被动/无源

 


- Digital 数字

 


- Analog 模拟

 

- RF 射频

 


 Electrical circuits for different application purposes



Boolean logic

- George Boole
(1815 - 1864)

 


- Values


- Boolean algebra allows only two values—0 and 1
- The beauty of the *digital abstraction* is that digital designers can focus on 1's and 0's, ignoring whether the Boolean variables are physically represented with specific voltages, rotating gears, etc.

- Basic operations

 - AND (conjunction) 与 xy
- OR (disjunction) 或 $x + y$
- NOT (negation) 非 \bar{x}



$x \wedge y$

 

$x \vee y$



$\neg x$


Logic 0	Logic 1
False	True
Off	On
LOW	HIGH
No	Yes
Open switch	Closed switch

x	y	$x \wedge y$	$x \vee y$	x	$\neg x$
0	0	0	0	0	1
1	0	0	1	1	0
0	1	0	1		
1	1	1	1		

Basic logic gates

- NOT gate
- OR gate
- AND gate


NOT

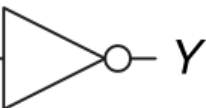

$Y = \bar{A}$

A	Y
0	1
1	0


OR



$Y = A + B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


AND



$Y = AB$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

AND4




$Y = ABCD$

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

- Buffer



BUF

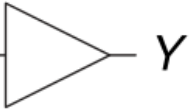


$Y = A$

A	Y
0	0
1	1


Logic gate implementation

  


• Mechanical way

 

• Electrical way

 


Schematic

 


Physical layout

A 3D-view of the CMOS implementation


INVERTER

 


Input	Output
1	0
0	1

 


Top View

 


3D View

 


Side View

 


1. Grow field oxide

 

2. Etch oxide for pMOSFET

 


3. Diffuse n-well

 

4. Etch oxide for nMOSFET




5. Grow gate oxide

 

6. Deposit polysilicon



7. Etch polysilicon and oxide

 

8. Implant sources and drains



9. Grow nitride



10. Etch nitride




11. Deposit metal



12. Etch metal



13. Etch metal

 


14. Etch metal




CMOS implementation of a buffer

• Why we need a buffer?

- Logical (virtual) representation

 


- Physical implementation

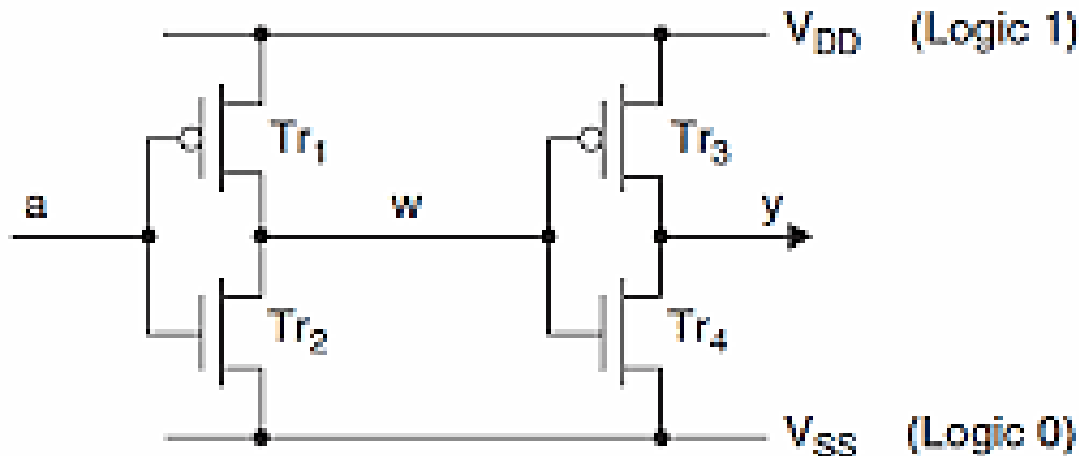


- From the logical point of view, a buffer might seem useless 逻辑上没有意义
- From the analog point of view, the buffer might have desirable characteristics such as the ability to **deliver large amounts of current** to **drive** a motor or many gates 物理上增强驱动能力
- This is an example of why we **need to consider multiple levels of abstraction** to fully understand a system; the digital abstraction hides the real purpose of a buffer.

The physical considerations

- Noise margins

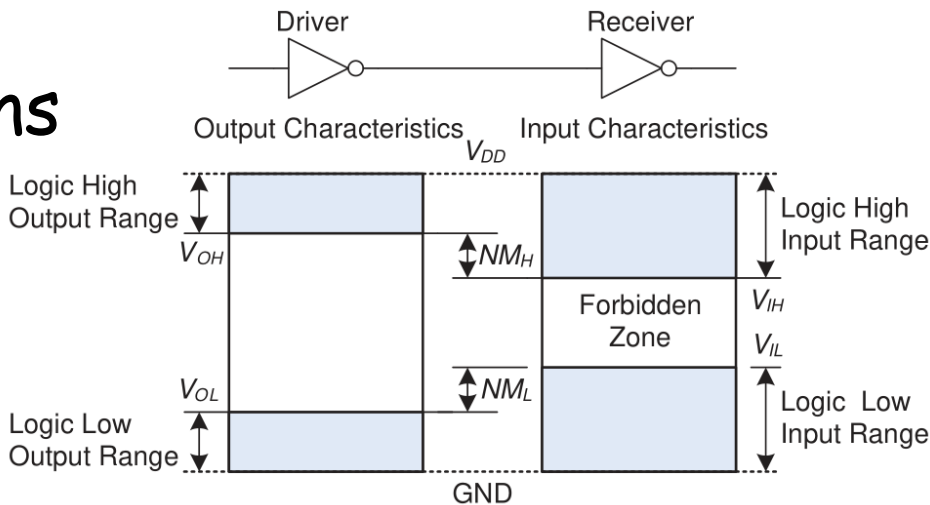


- DC transfer characteristics

 


- Physical chip



2 Input NAND Gate

 

 - A digital clock built with 74LSxx chips



Other logic gates

异或门

XOR



$Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

与非门

NAND



$Y = \overline{AB}$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

或非门

NOR




$Y = \overline{A + B}$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

同或门

XNOR

 

$Y = \overline{A \oplus B}$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

三输入或非门

NOR3




$Y = \overline{A + B + C}$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


Digital electronics

- Combinational logic circuit

 

- Output depends on
 - Present input values
- No memory

- Sequential logic circuit

 


- Output depends on
 - Present inputs
 - The history of past inputs
- Have memory

Circuit implementation



- 3 input majority function
 - Truth table

S1	S2	S3	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

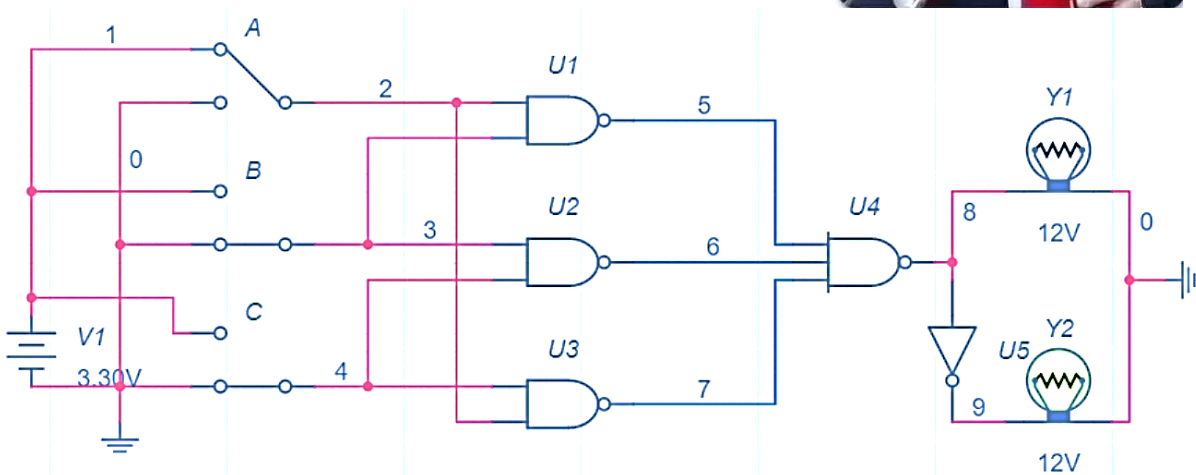

- Logic expression

$$Y = AB + BC + AC$$

$$= \overline{\overline{AB}} \overline{\overline{BC}} \overline{\overline{AC}}$$

Boolean algebra

• Axioms 公理

Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

• Theorems of two variables

Theorem		Dual		Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + (B \bullet D) = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D) = B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D) = (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots} = (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots)$	De Morgan's Theorem

• Theorems of one variable

Theorem		Dual		Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

Generalized procedures of combinational circuit design

- Improved equation minimization

Step	Equation	Justification
	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	
1	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	T3: Idempotency
2	$\overline{B} \overline{C}(\overline{A} + A) + A \overline{B}(\overline{C} + C)$	T8: Distributivity
3	$\overline{B} \overline{C}(1) + A \overline{B}(1)$	T5: Complements
4	$\overline{B} \overline{C} + A \overline{B}$	T1: Identity

- Sum of product 积(与)的和(或)
(Multiple AND terms ORed together)

- 1. $ABC + \overline{A} \overline{B} \overline{C}$
- 2. $AB + \overline{A} \overline{B} \overline{C} + \overline{C} \overline{D} + D$
- 3. $\overline{A} B + \overline{C} \overline{D} + EF + GK + H \overline{L}$

- Product of sum 和(或)的积(与)
(Multiple OR terms ANDed together)

- 1. $(A + \overline{B} + C)(A + C)$
- 2. $(A + \overline{B})(\overline{C} + D)F$
- 3. $(A + C)(B + \overline{D})(\overline{B} + C)(A + \overline{D} + \overline{E})$

Generalized procedures of combinational circuit design

- Interpret the problem and set up its **truth table**
- Write the **AND** (product) **term** for each case where output = 1
- Combine the terms in **SOP** (sum of product) form
- **Simplify** the output expression if possible
- Implement the **circuit** for the final, simplified expression

- Equation minimization example

Step	Equation	Justification
	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	
1	$\overline{B} \overline{C}(\overline{A} + A) + A \overline{B} C$	T8: Distributivity
2	$\overline{B} \overline{C}(1) + A \overline{B} C$	T5: Complements
3	$\overline{B} \overline{C} + A \overline{B} C$	T1: Identity

Karnaugh map (K-maps)



- A graphical method for simplifying Boolean equations
 - Invented in 1953 by **Maurice Karnaugh** at Bell Labs
 - Adjacent squares share all the same literals **except one**
相邻格的输入值**仅有一位**变化
 - The K-map also "**wraps around.**"
左右环接

		BC			
		00	01	11	10
A	0	1	0	1	1
	1	1	0	0	1

- Rules for finding a minimized equation:
 - Use the **fewest circles** necessary to cover all the 1's.
 - All the squares in each circle **must contain 1's**.
 - Each circle must span a **rectangular block** that is a power of 2 (i.e., 1, 2, or 4) squares in each direction.
 - Each circle should be **as large as possible**.
 - A circle may **wrap around** the edges of the K-map.
 - A 1 in a K-map **may be circled multiple times** if doing so allows fewer circles to be used.

Example: 7-segment decoder

- 7-segment display

  

(Pictures are from the Internet)


- Truth table

binary-coded decimal (BCD)


$D_{3:0}$	S_a	S_b	S_c	S_d	S_e	S_f	S_g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1
others	0	0	0	0	0	0	0

Example: 7-segment decoder

- K-map solution of S_a

 

Alternative
K-map

 

- Truth table

$D_{3:0}$	S_a	S_b	S_c	S_d	S_e	S_f	S_g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1
others	0	0	0	0	0	0	0

- Result & circuit

